

Drone

# Controller


• capacitor (10uF)

• VCC

• GND

• digital

• analog

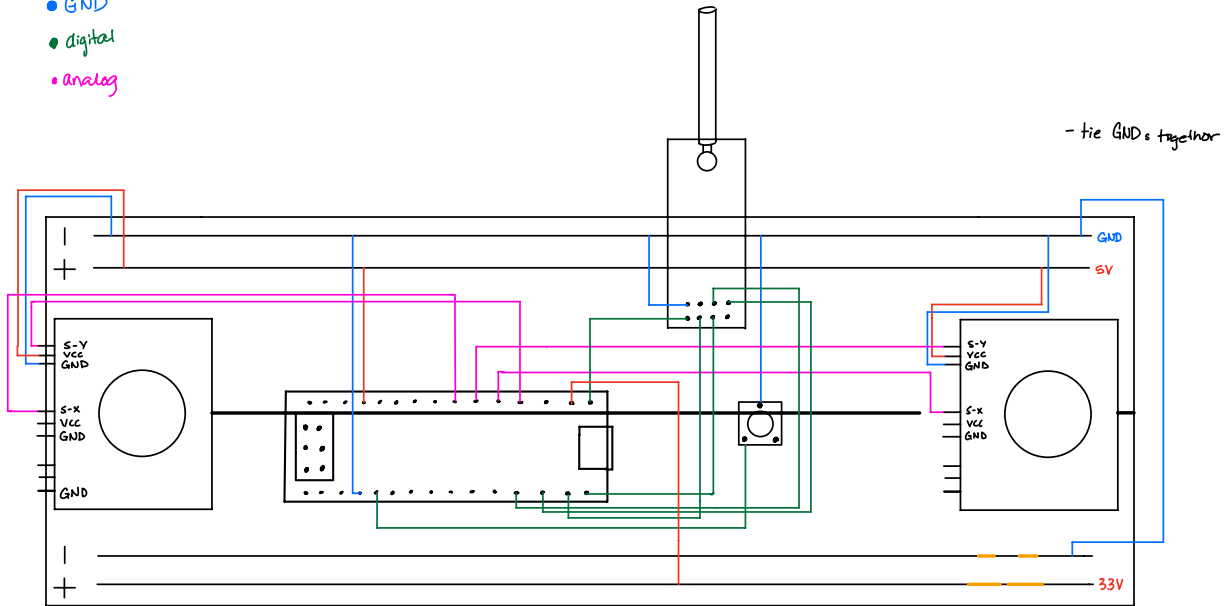

## Parts:

- Joystick (2)
- nrf6050 (1)
- button (1) (pulled up)
- Arduino Nano (1)

- button doesn't need power; it just breaks the connection when disarmed

nrf module : GND VCC CE CSW  
 has to be SCK MISO MISO IRQ  
 3.3V